

Task 2

Starting with the following function expressed in maxterms:

$$f(d, c, b, a) = \prod (M_0, M_1, M_5, M_7, M_8, M_{10}, M_{14}, M_{15})$$

Taking d, c, b, a as input variables. For simplify, the same function is expressed in minterms to operate later:

$$f(d, c, b, a) = \sum (m_2, m_3, m_4, m_6, m_9, m_{11}, m_{12}, m_{13})$$

Starting with it, we build the function without simplifying:

$$f(d, c, b, a) = (\bar{d} \cdot \bar{c} \cdot b \cdot \bar{a}) + (\bar{d} \cdot \bar{c} \cdot b \cdot a) + (\bar{d} \cdot c \cdot \bar{b} \cdot \bar{a}) + (\bar{d} \cdot c \cdot b \cdot \bar{a}) + (d \cdot \bar{c} \cdot \bar{b} \cdot a) + (d \cdot \bar{c} \cdot b \cdot a) + (d \cdot c \cdot \bar{b} \cdot \bar{a}) + (d \cdot c \cdot \bar{b} \cdot a)$$

We grouped by common factor in a convenient way:

$$\begin{aligned} f(d, c, b, a) &= \underbrace{(\bar{d} \cdot \bar{c} \cdot b \cdot \bar{a}) + (\bar{d} \cdot \bar{c} \cdot b \cdot a)}_{(d \cdot c \cdot \bar{b} \cdot \bar{a}) + (d \cdot c \cdot \bar{b} \cdot a)} + \underbrace{(\bar{d} \cdot c \cdot \bar{b} \cdot \bar{a}) + (\bar{d} \cdot c \cdot b \cdot \bar{a})}_{(d \cdot c \cdot \bar{b} \cdot \bar{a}) + (d \cdot c \cdot \bar{b} \cdot a)} + \underbrace{(d \cdot \bar{c} \cdot \bar{b} \cdot a) + (d \cdot \bar{c} \cdot b \cdot a)}_{(d \cdot \bar{c} \cdot \bar{b} \cdot a) + (d \cdot \bar{c} \cdot b \cdot a)} \\ &\rightarrow \underbrace{(d \cdot c \cdot \bar{b} \cdot \bar{a}) + (d \cdot c \cdot \bar{b} \cdot a)}_{(d \cdot c \cdot \bar{b} \cdot \bar{a}) + (d \cdot c \cdot \bar{b} \cdot a)} \end{aligned}$$

$$f(d, c, b, a) = [\bar{d} \cdot \bar{c} \cdot b \cdot \underbrace{(\bar{a} + a)}_1] + [\bar{d} \cdot c \cdot \bar{a} \cdot \underbrace{(\bar{b} + b)}_1] + [d \cdot \bar{c} \cdot a \cdot \underbrace{(\bar{b} + b)}_1] + [d \cdot c \cdot \bar{b} \cdot \underbrace{(\bar{a} + a)}_1]$$

$$f(d, c, b, a) = (\bar{d} \cdot \bar{c} \cdot b) + (\bar{d} \cdot c \cdot \bar{a}) + (d \cdot c \cdot \bar{b}) + (d \cdot \bar{c} \cdot a)$$

Analogously, starting with the expression in minterms we reduce the function through a map of Karnaugh:

		ba			
		00	01	11	10
dc	00	0	0	1	1
	01	1	0	0	1
	11	1	1	0	0
	10	0	1	1	0

From the first group (first row) we have that d, c and b are constantes, thus the first factor stays the way $\bar{d}\bar{c}b$.

From the second group (second row) we have d, c and a as constants, thus this factor stays as $\bar{d}c\bar{a}$.

From the third group (third row) remain constant d, c and b , thus this factor stays as $d\bar{c}\bar{b}$.

Finally, from the last row, in the group d, c and a stay constant, thus this factor stays the way $d\bar{c}a$.

Adding the partial termns we get the simplified function:

$$f(d, c, b, a) = (\bar{d} \cdot \bar{c} \cdot b) + (\bar{d} \cdot c \cdot \bar{a}) + (d \cdot c \cdot \bar{b}) + (d \cdot \bar{c} \cdot a)$$

Wich is the same obtained by simplification by boolean algebra.

Taking this function, it was implemented in a logical circuit by AND, OR and NOT gates, as shown below.

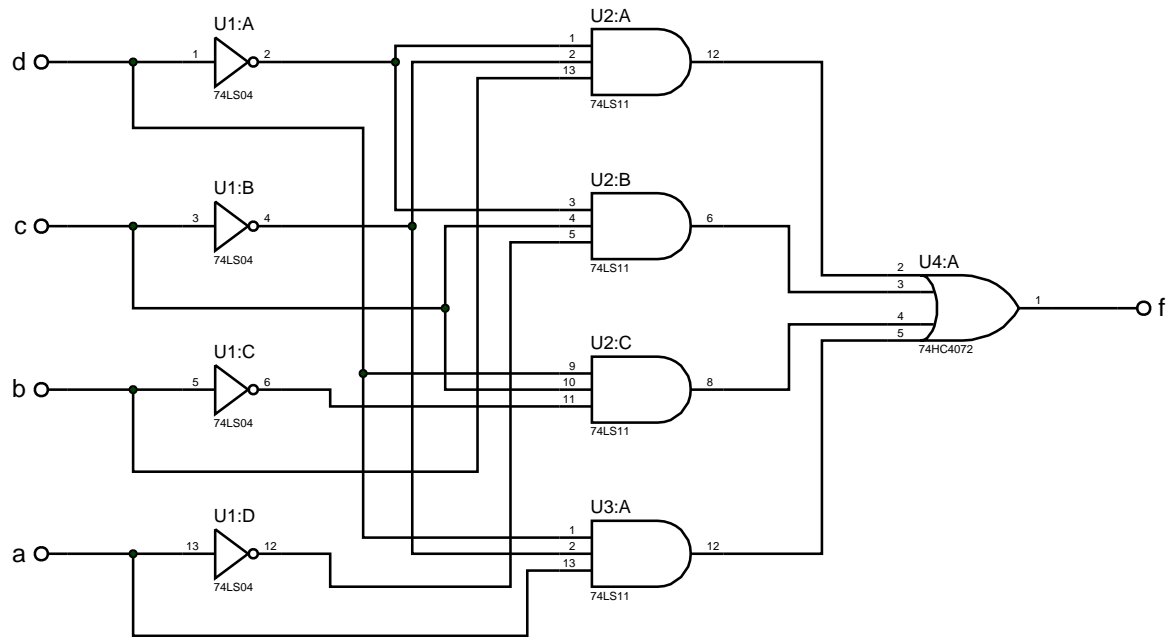


Figure 1: Logical circuit that implements $f(d, c, b, a)$ - Made in Proteus 7.8

For implementation using only NOR gates, first we have to work with the obtained function applying boolean algebra properties. Taking the function:

$$f(d, c, b, a) = (\bar{d} \cdot \bar{c} \cdot b) + (\bar{d} \cdot c \cdot \bar{a}) + (d \cdot c \cdot \bar{b}) + (d \cdot \bar{c} \cdot a)$$

We twice denied the terms separated by sums, for keeping the equal:

$$f(d, c, b, a) = \overline{\overline{(\bar{d} \cdot \bar{c} \cdot b)}} + \overline{\overline{(\bar{d} \cdot c \cdot \bar{a})}} + \overline{\overline{(d \cdot c \cdot \bar{b})}} + \overline{\overline{(d \cdot \bar{c} \cdot a)}}$$

Next we deny the factors only once, for turning the products into sums (property of De Moivre):

$$f(d, c, b, a) = \overline{(d + c + \bar{b})} + \overline{(d + \bar{c} + a)} + \overline{(\bar{d} + c + b)} + \overline{(\bar{d} + c + \bar{a})}$$

Having the expression in terms of sums, it is possible to implement the circuit using only NOR gates, as shown below.

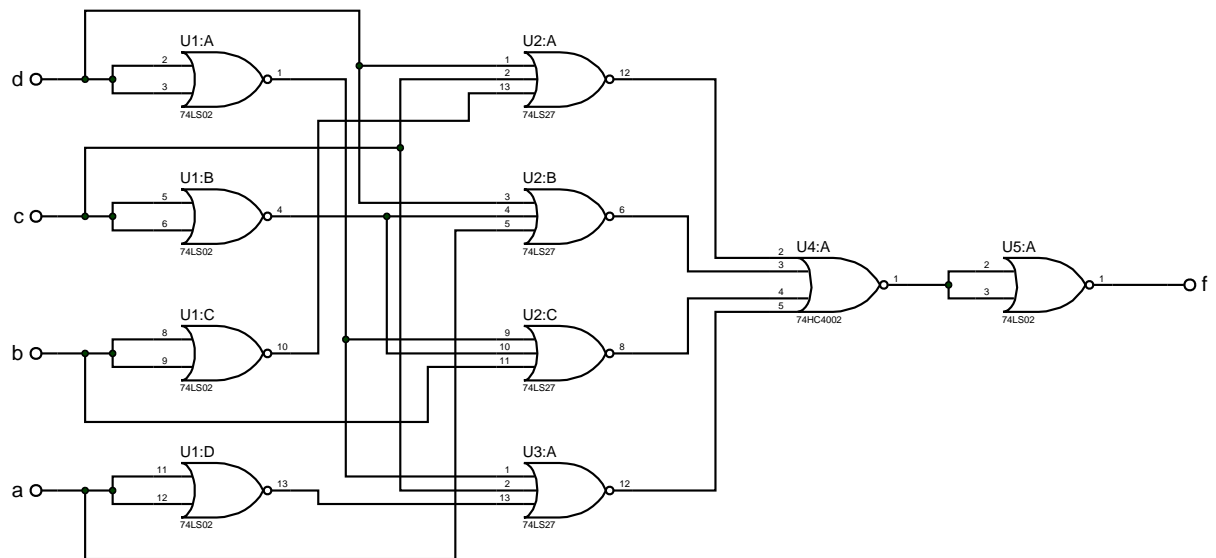


Figure 2: Logical circuit that implements $f(d, c, b, a)$ with NOR gates - Made in Proteus 7.8